

CS-200


Computer Architecture

Part 2a. I/Os & Exceptions


Multicycle Processor

Paolo Ienne
<paolo.ienne@epfl.ch>

The Contract between HW and SW

 


The Processor

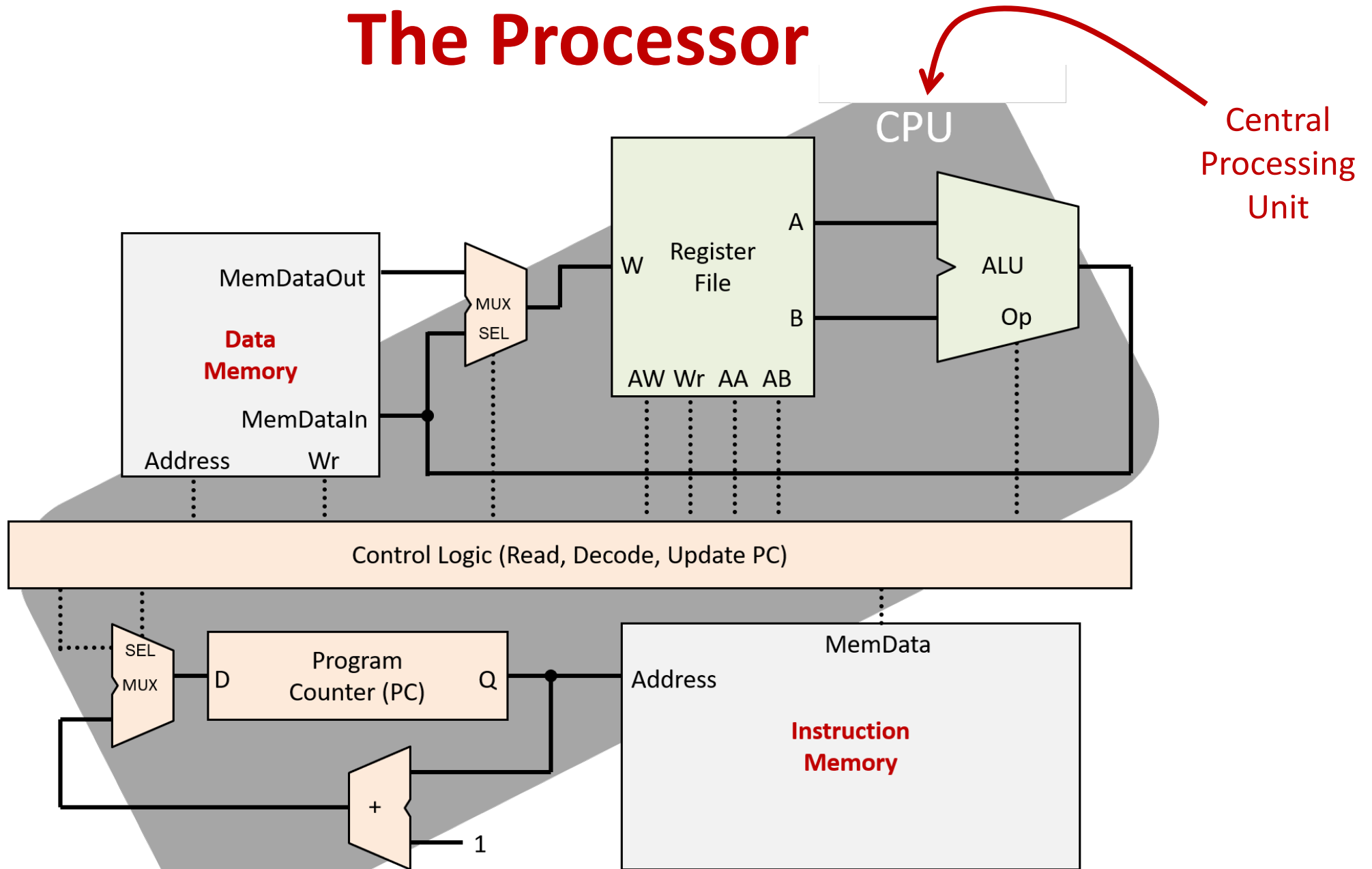





A Big Finite-State Machine

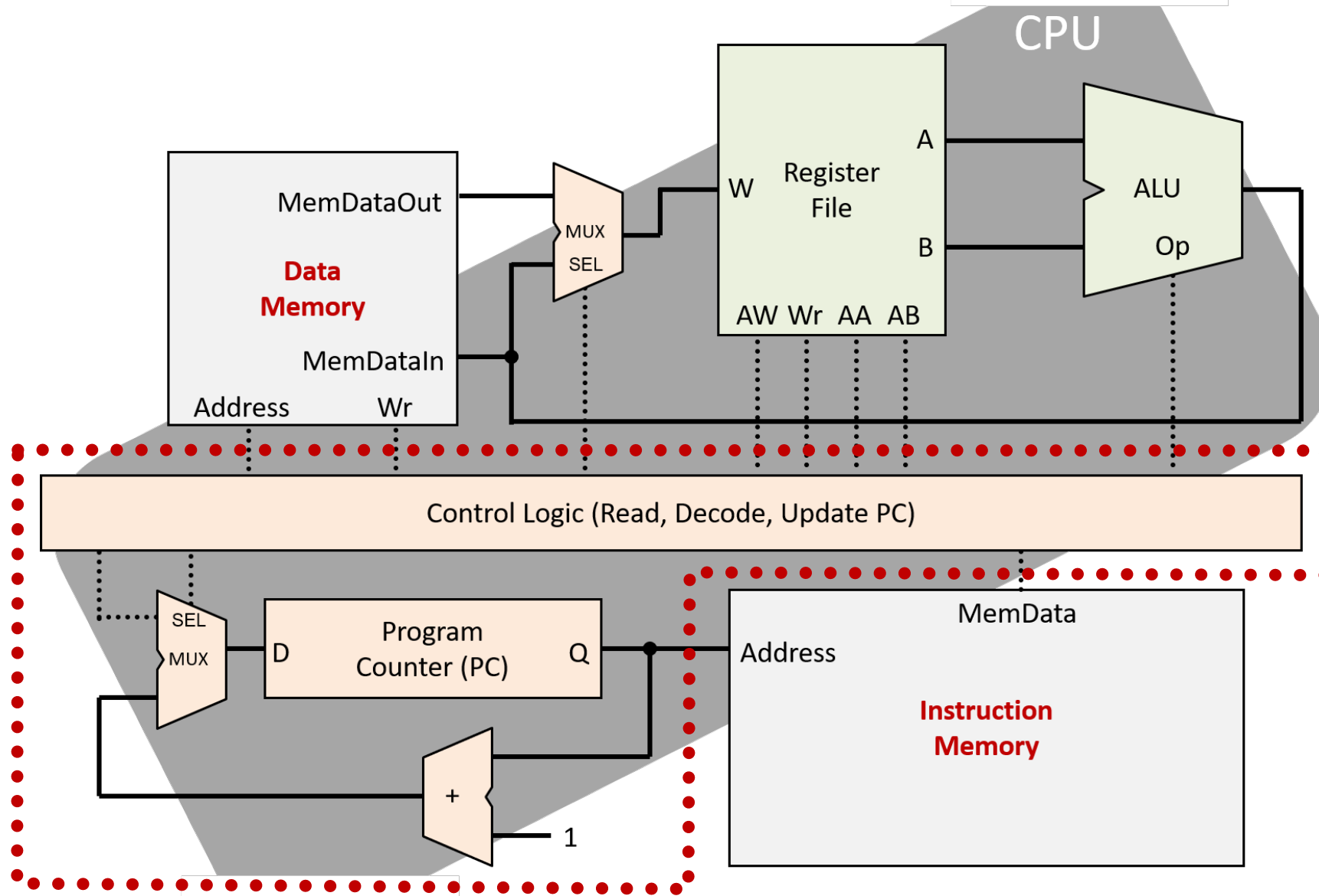


Single-Cycle Processor

 

Propagation Time

 

Increasing the Frequency?

 


Two-Cycle Processor


Did we gain anything?

1 instruction **per cycle**
at frequency **F**


 
1 instruction
every **two cycles**
at frequency **2F**




Not All Paths Are Born Equal!

 

And Maybe Memories Are Sequential

 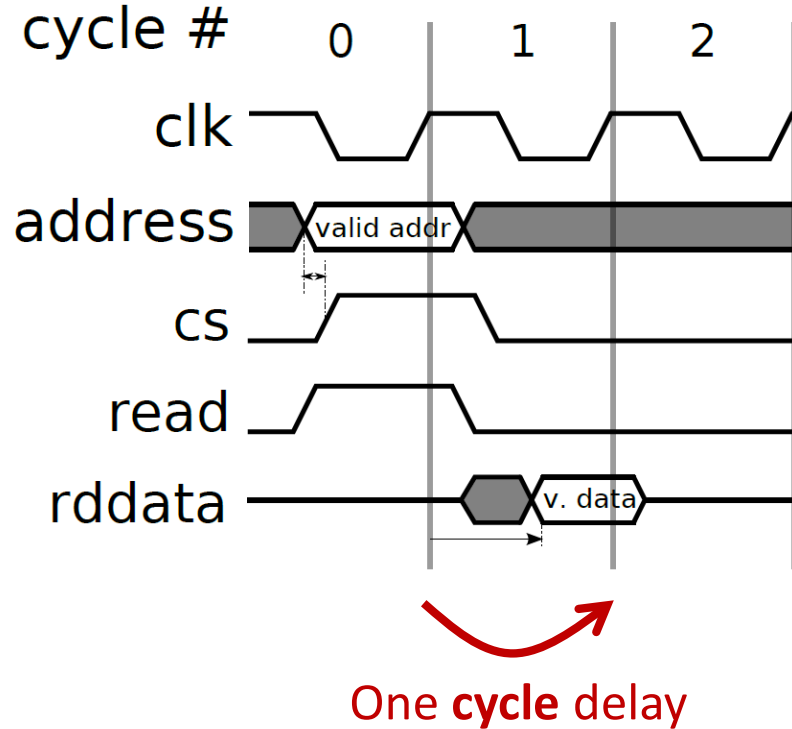


Multi-Cycle Processor

 


Get the
instruction
from memory

Multi-Cycle Processor

 


“Understand” the instruction and take a different path as needed (different resources to control, different complexity)

Multi-Cycle Processor

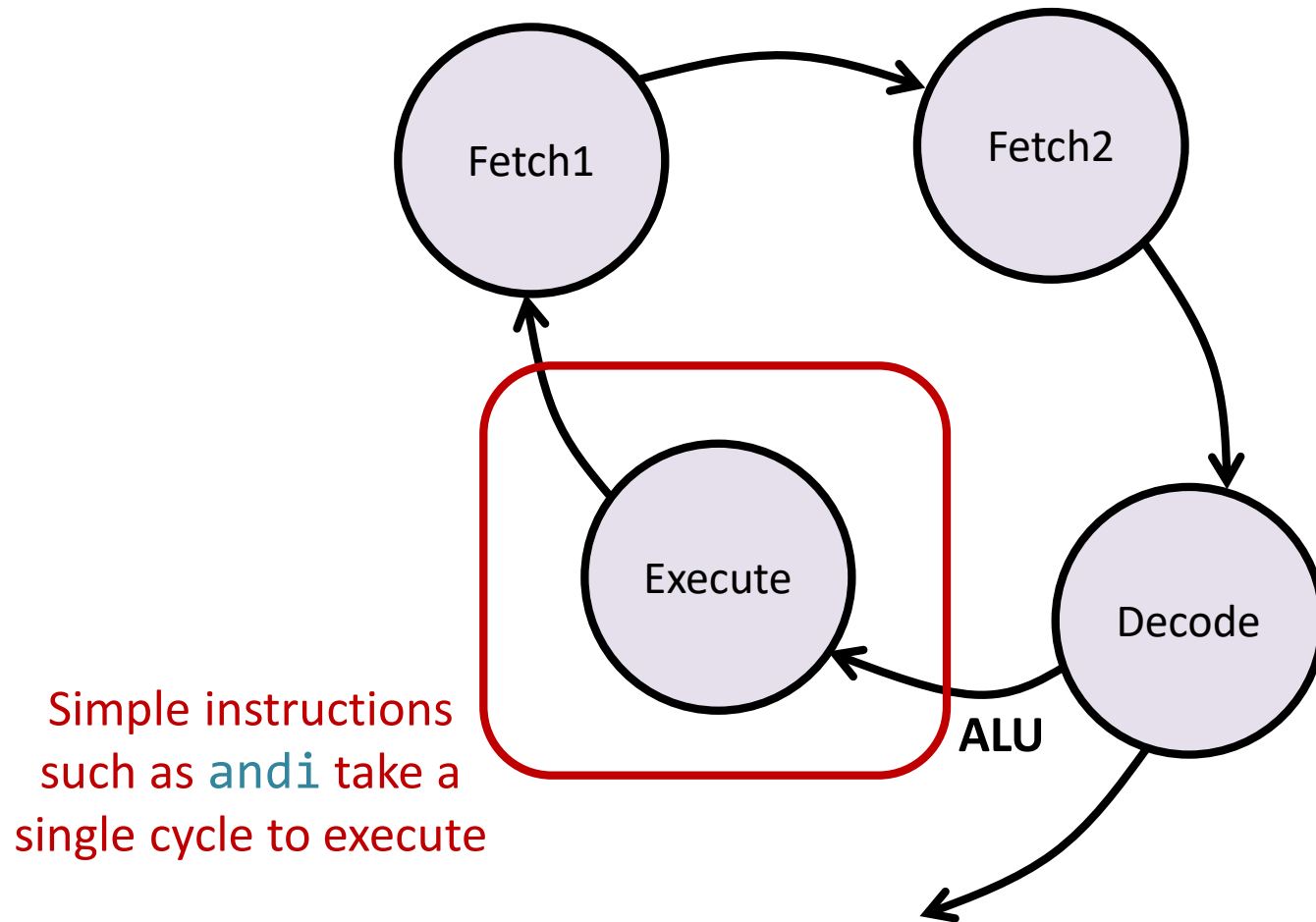


Multi-Cycle Processor

 


Complex ones such
as `lw` take longer

Multi-Cycle Processor

 


Mealy or Moore?

 

Mealy FSM

Output depends on
input and state

 

Moore FSM

Output depends on
state only

Sometimes
this needs
more cycles...

...and
sometimes
this is not
acceptable


Building the Circuit



An “empty” FSM
(we still do not know
what we need to control...)

Basic registers
we need


Add Progressively What We Need

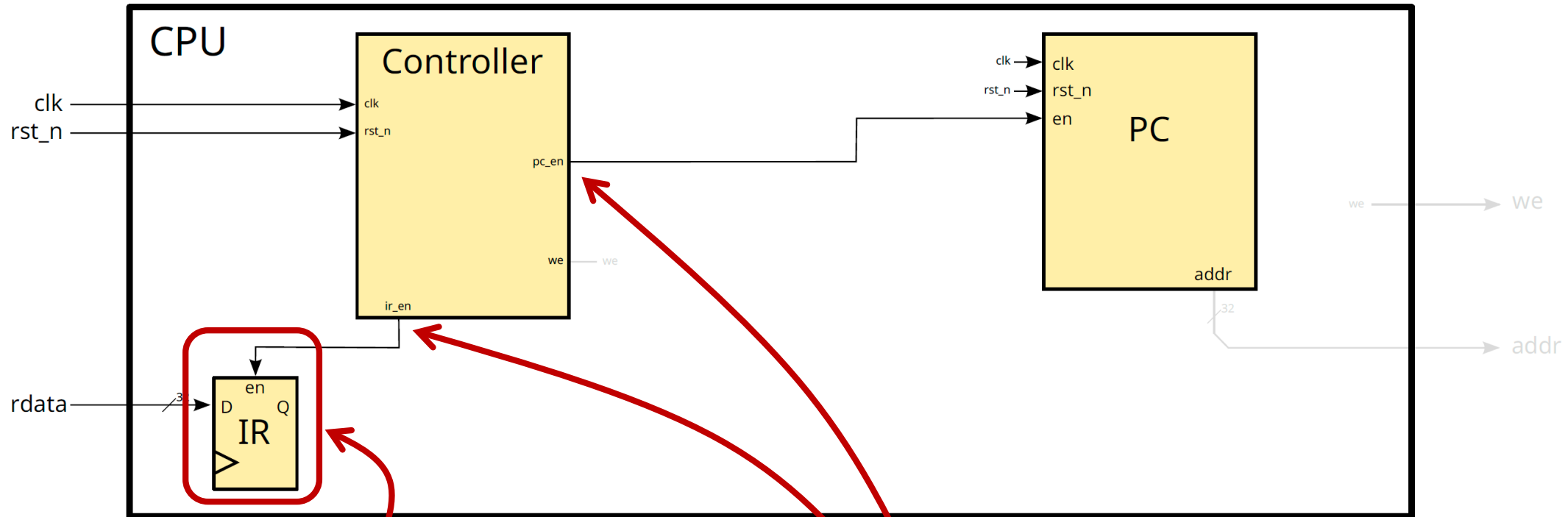

We will need an **Instruction Register** to memorize the instruction coming from memory

We will need to **enable** these registers when there is something new to record
→ we will have the **FSM generate them**


Follow the Functionality

 


When an instruction arrives into IR,
the controller needs to know what it is
(the next state depends on it!)
→ **connect IR to the controller**

I-Type Instructions Need RF and ALU


`addi t0, t1, 1234`

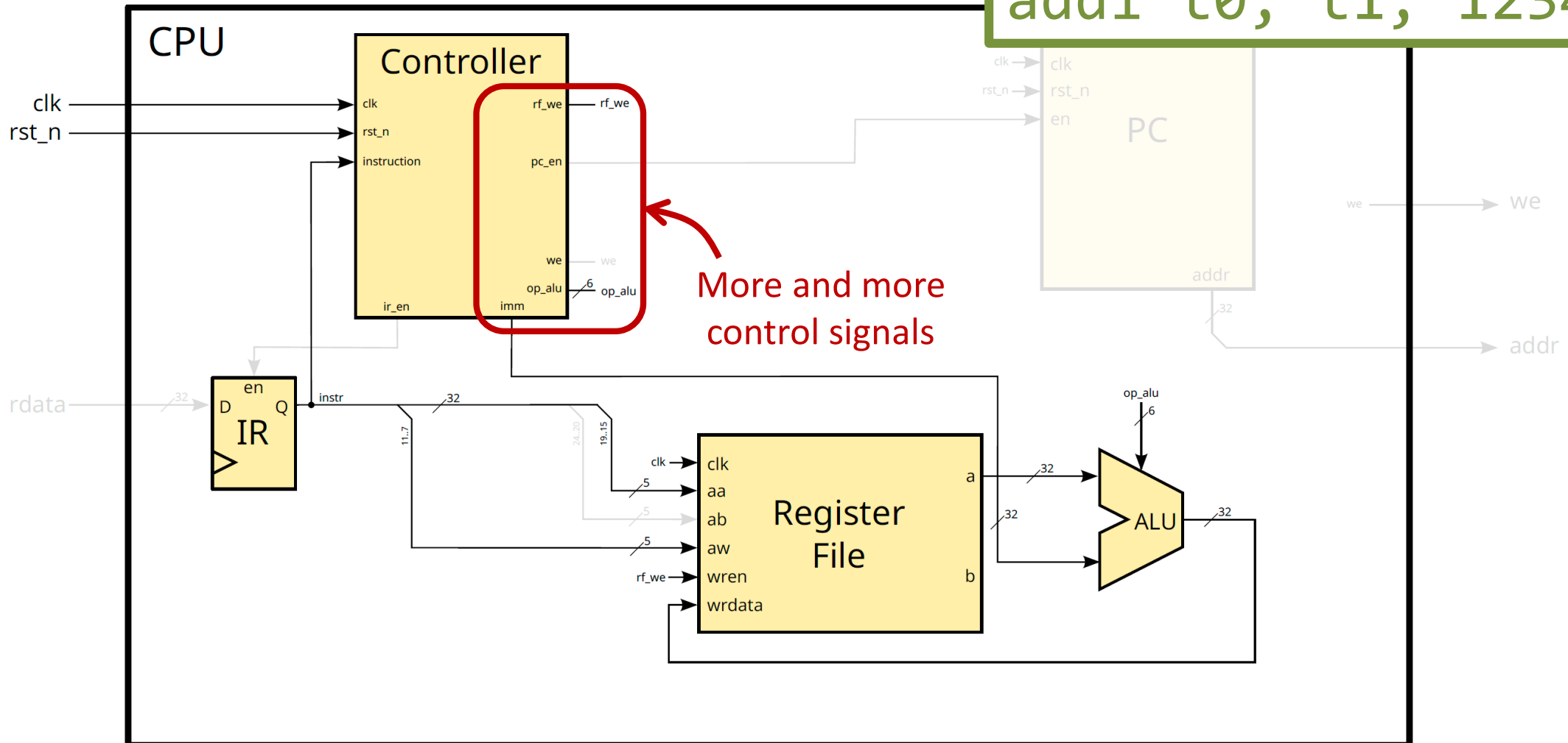


I-Type Instructions Need RF and ALU

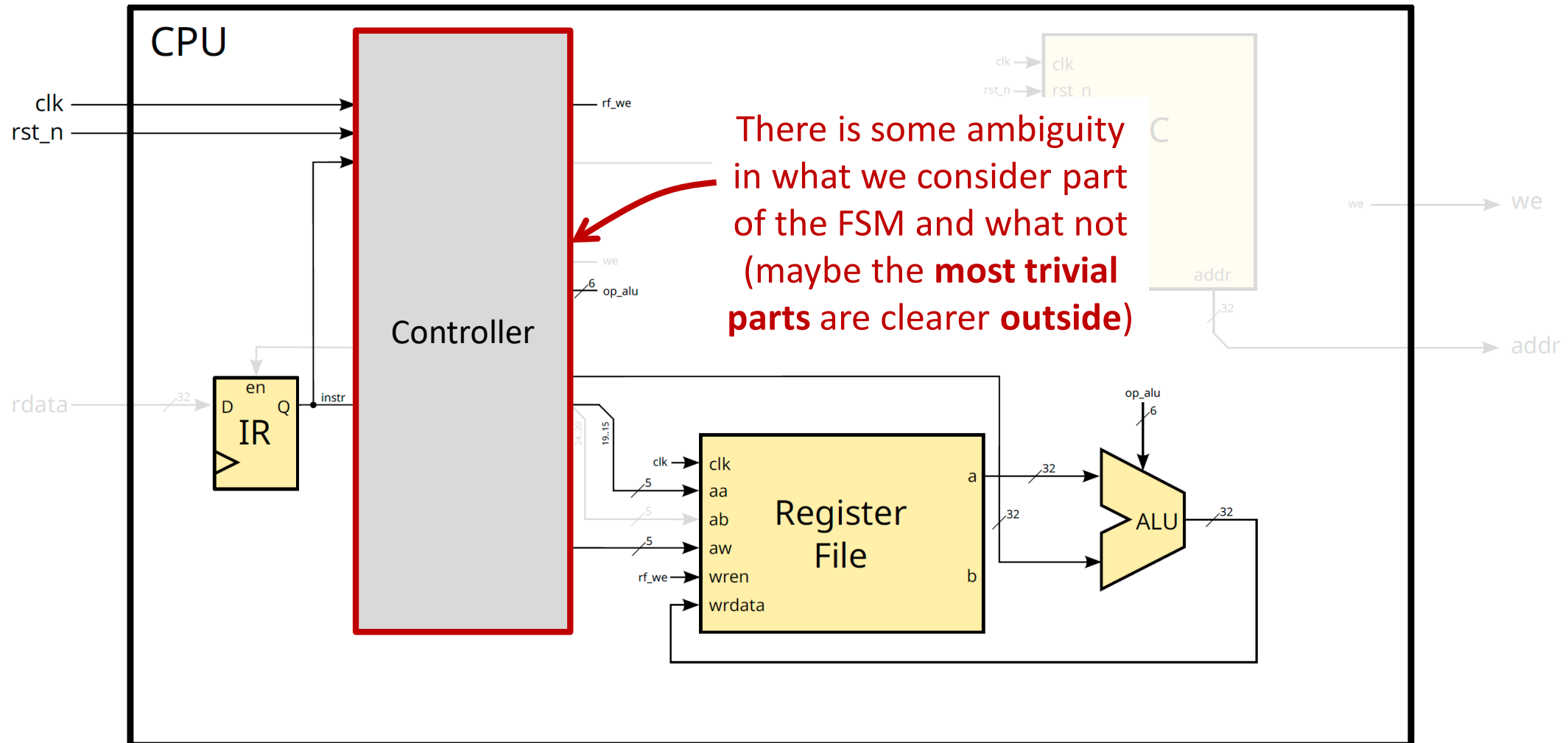

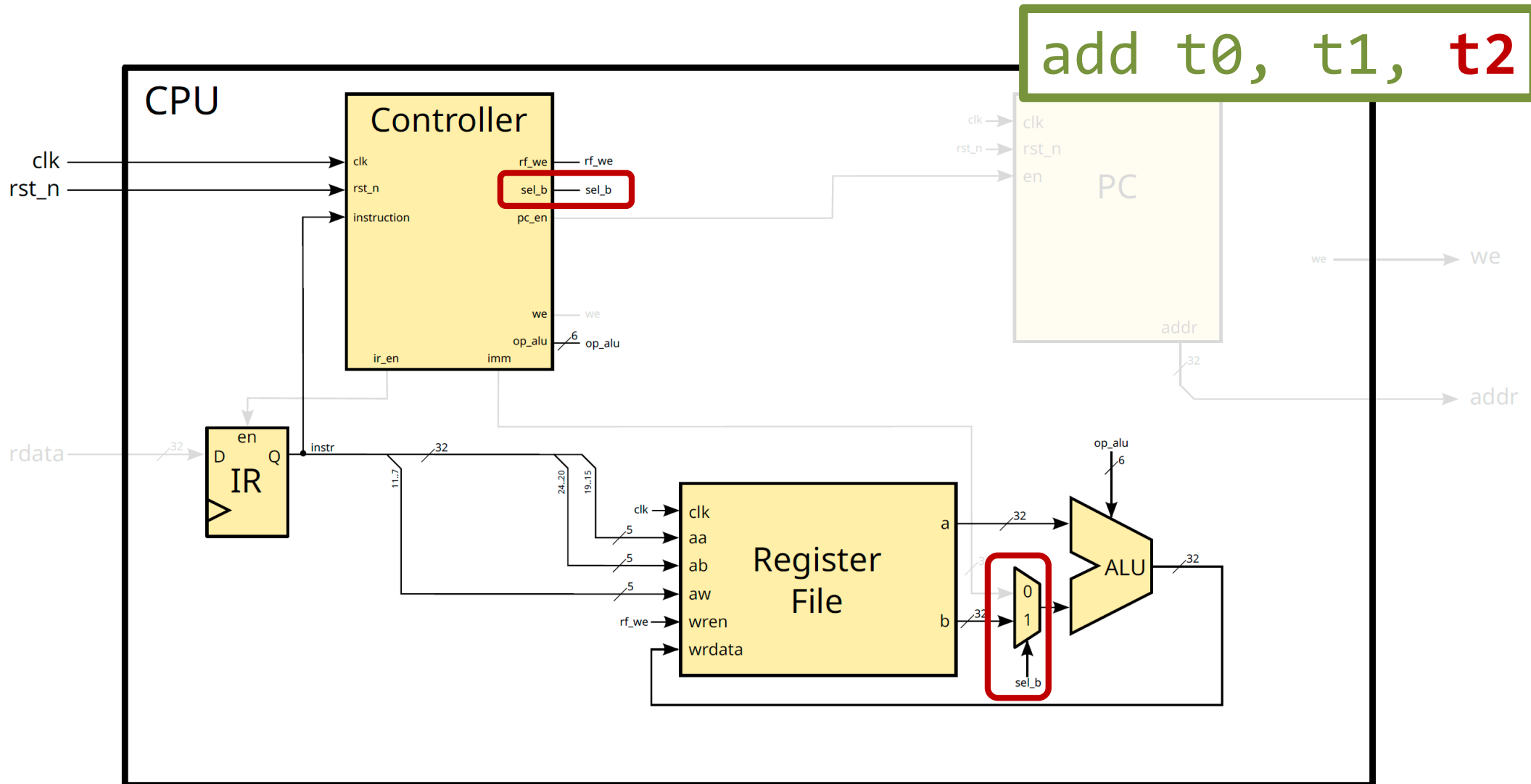
R-Type Instructions Need a Second Operand




U-Type Instructions Write an Immediate

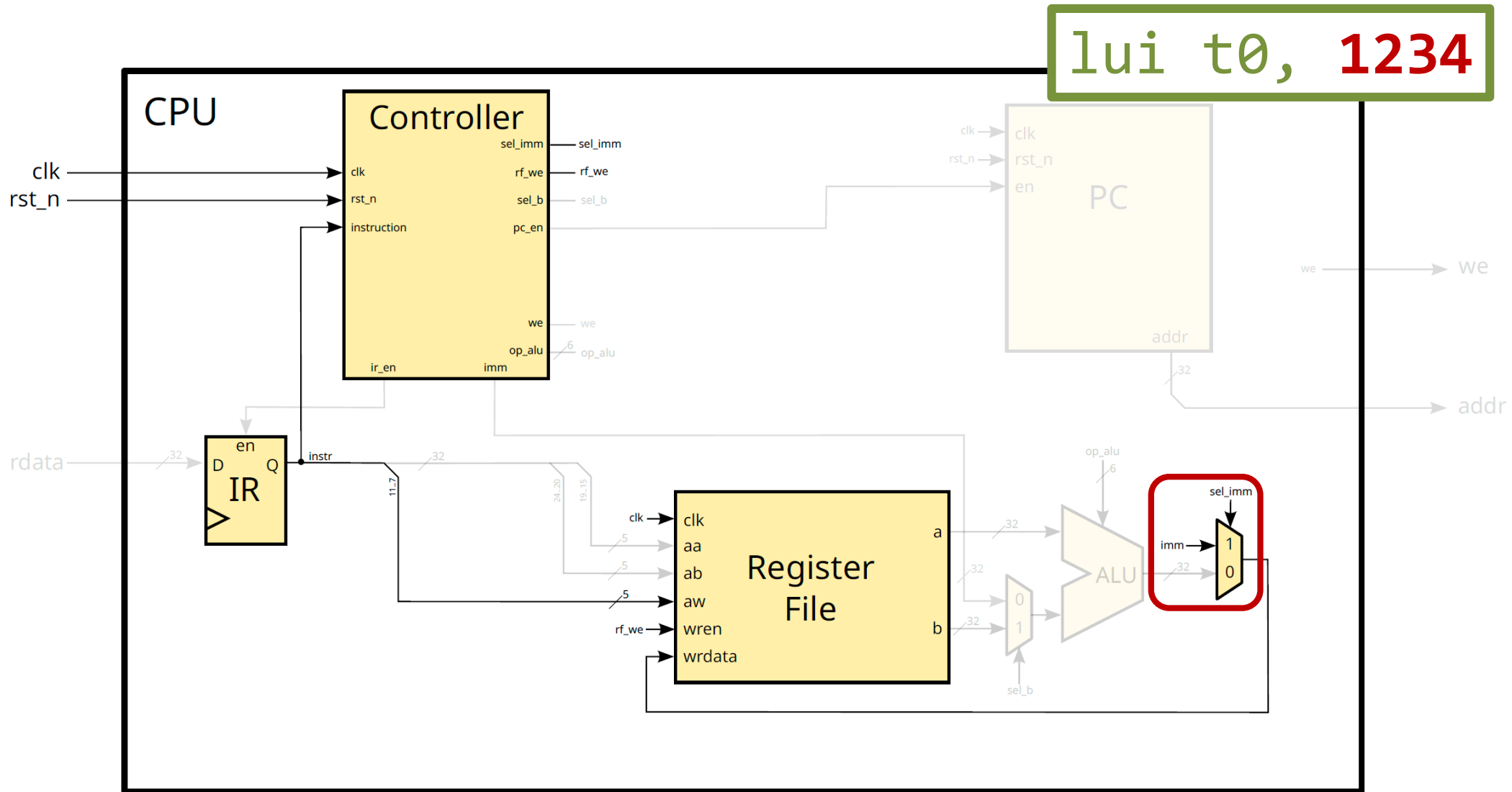


Load and Stores Produce a Memory Address

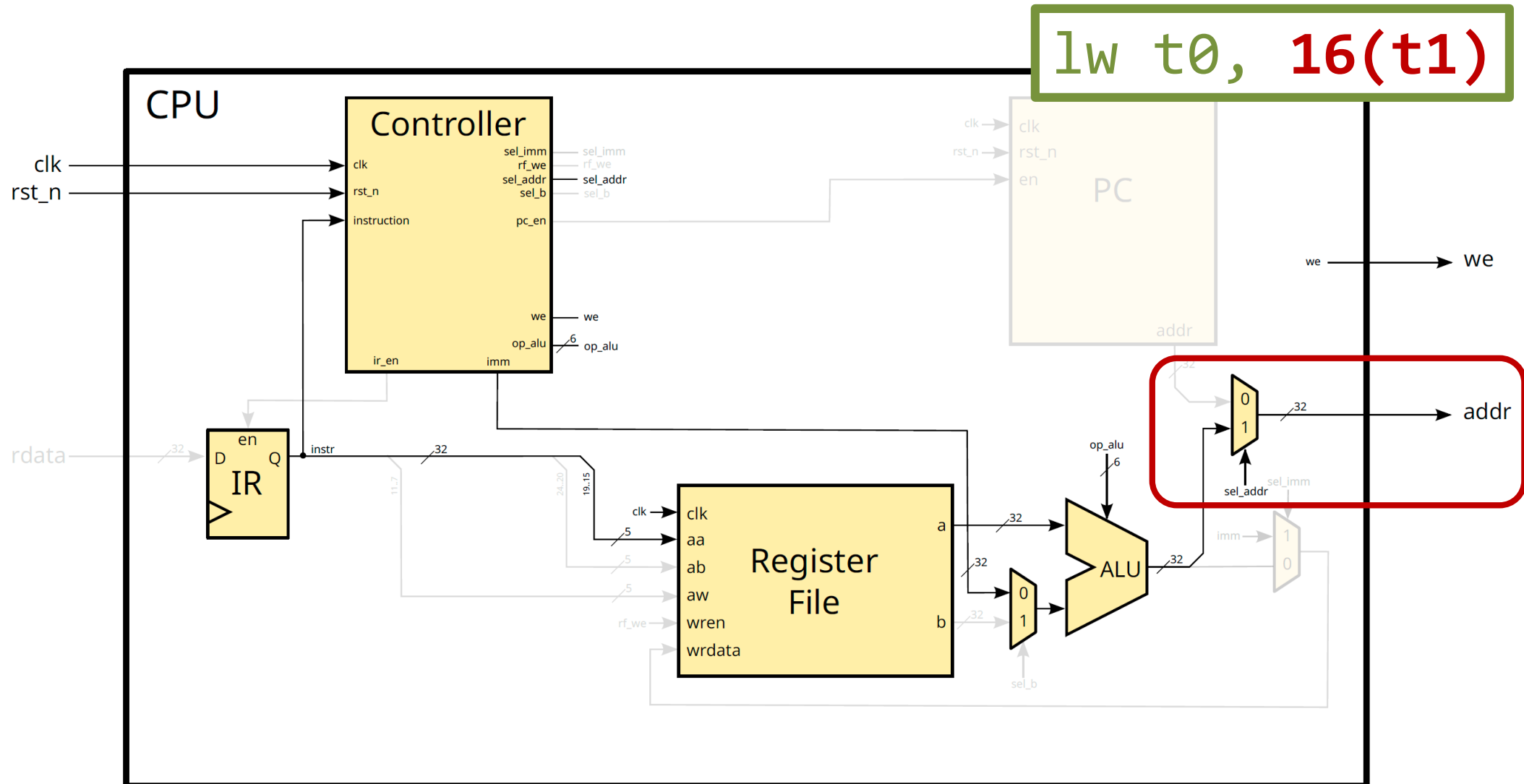


Loads Write the Read Data into the RF

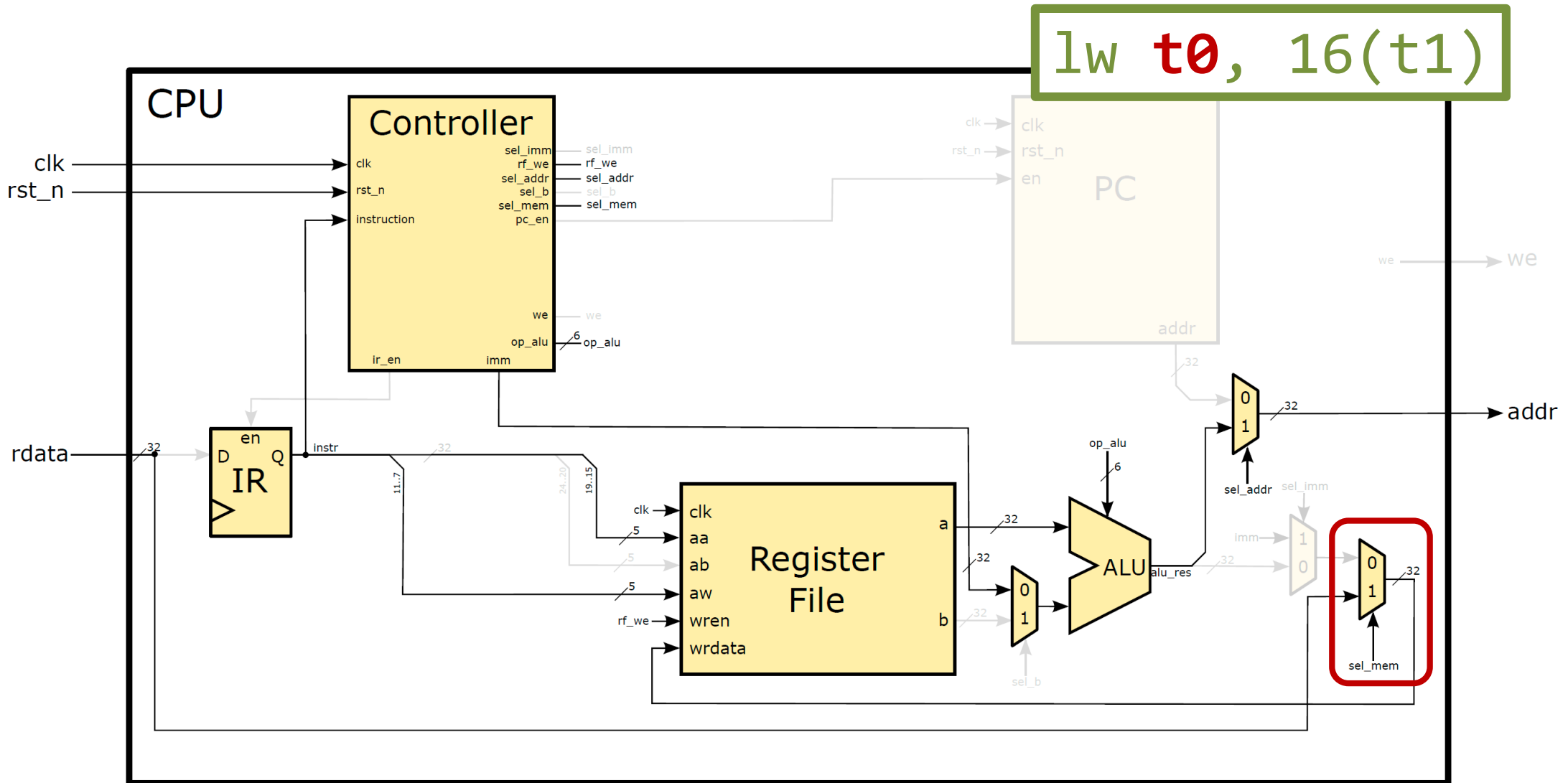

Stores Send an Operand to Memory

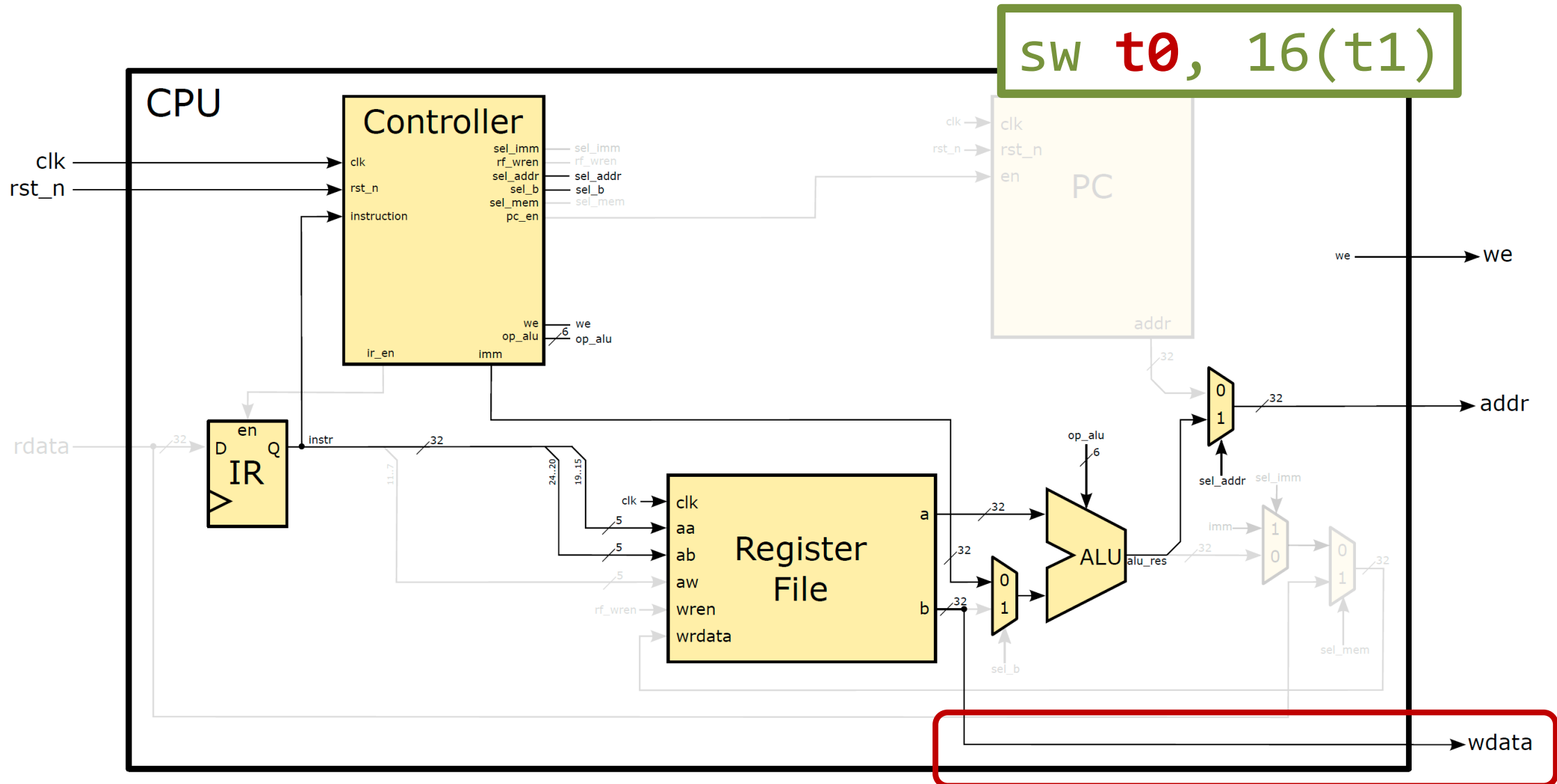


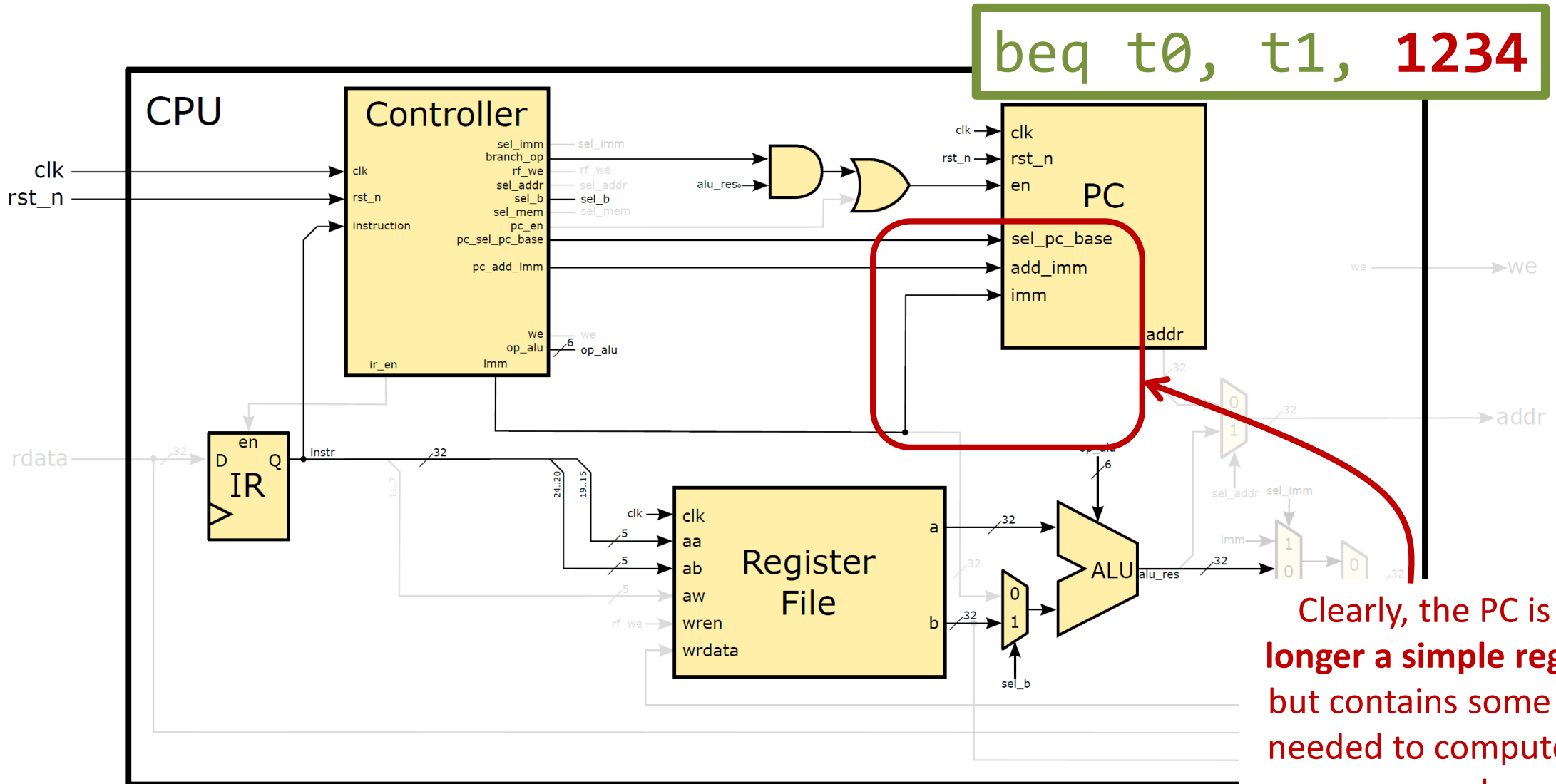Branches Need to Write an Offset to the PC




Clearly, the PC is **no longer a simple register** but contains some logic needed to compute the new value

jal Needs to Store PC + 4 in the RF

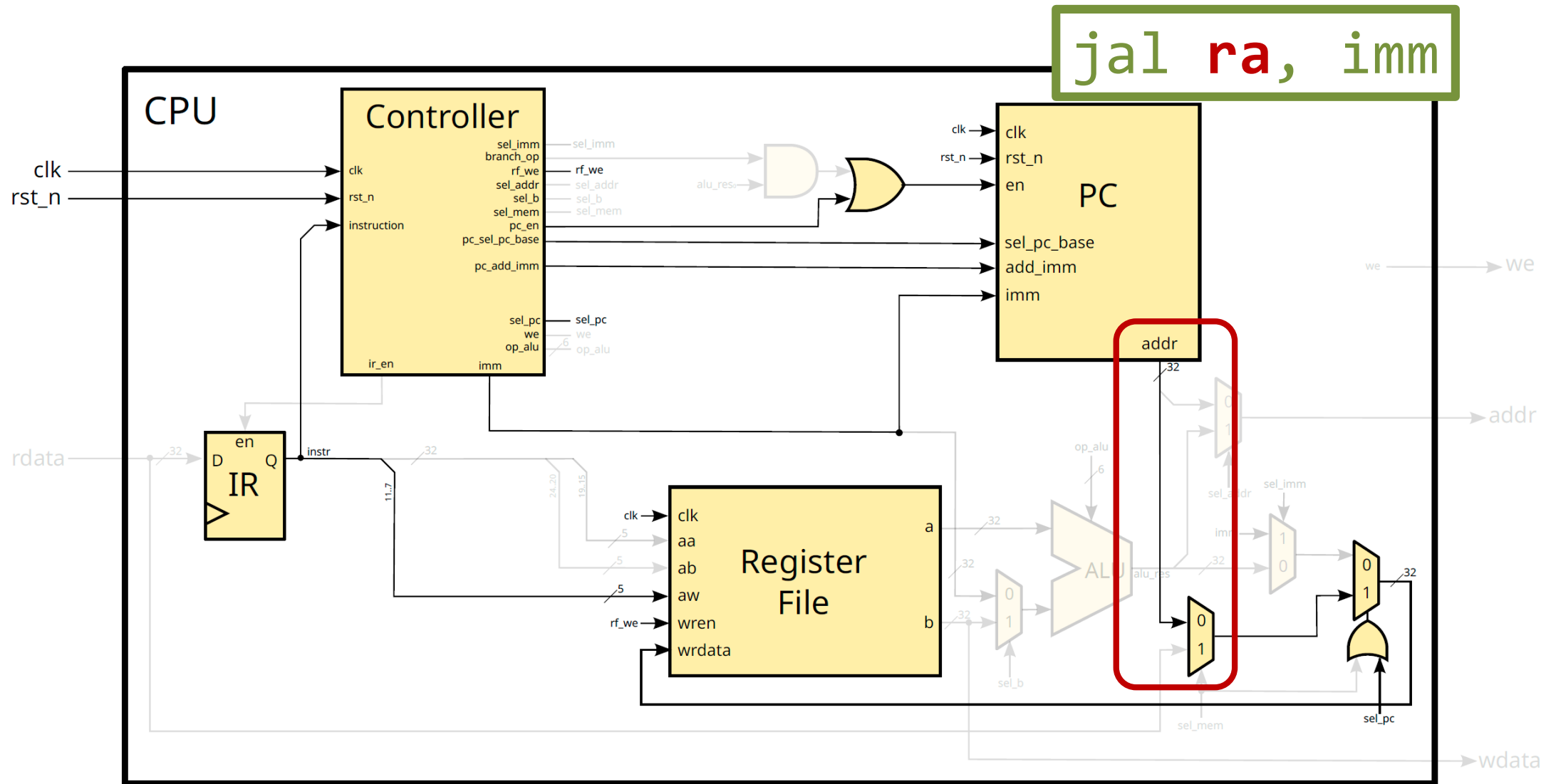

Jumps Need to Write an Address to the PC

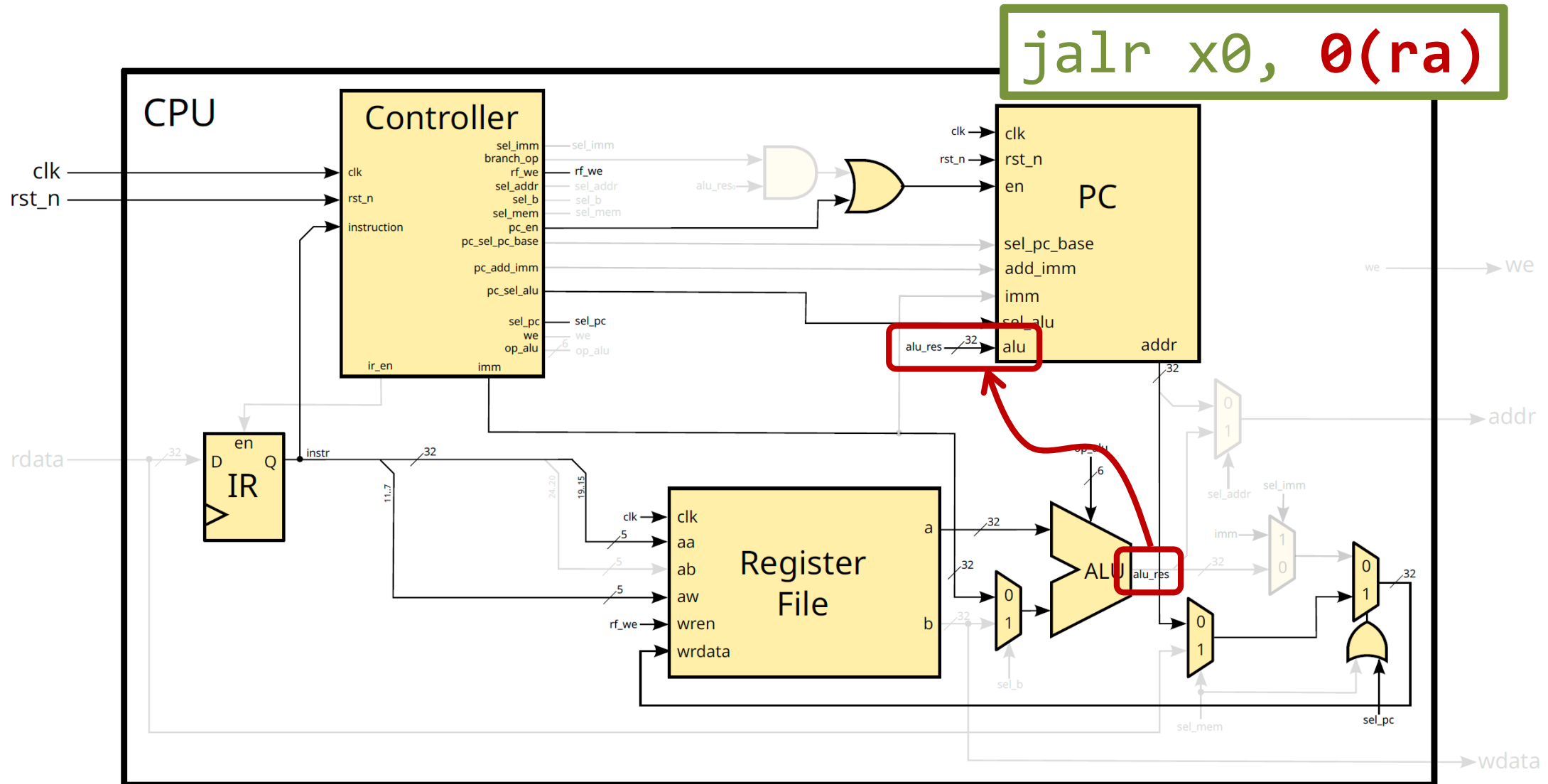


Do Not Write Verilog until Done!


- Verilog and VHDL are **HDLs** → Hardware **Description** Languages
- Describe something only when it is perfectly **clear**:
 - You have **drawn a diagram** like the one of the previous slide
 - You have clearly identified **combinational** and **sequential** blocks
- Always **decompose complex sequential** blocks
 - Describe **only** sequential blocks that are **simple registers** (e.g., IR)
 - Draw **hierarchical diagrams** until sequential blocks are trivial
- Use a **hierarchical approach** (much as in programming) and use your diagrams to guide the creation of modules (e.g., PC)

Write Only Simple Stuff






Formal FSM
→ Ready to write

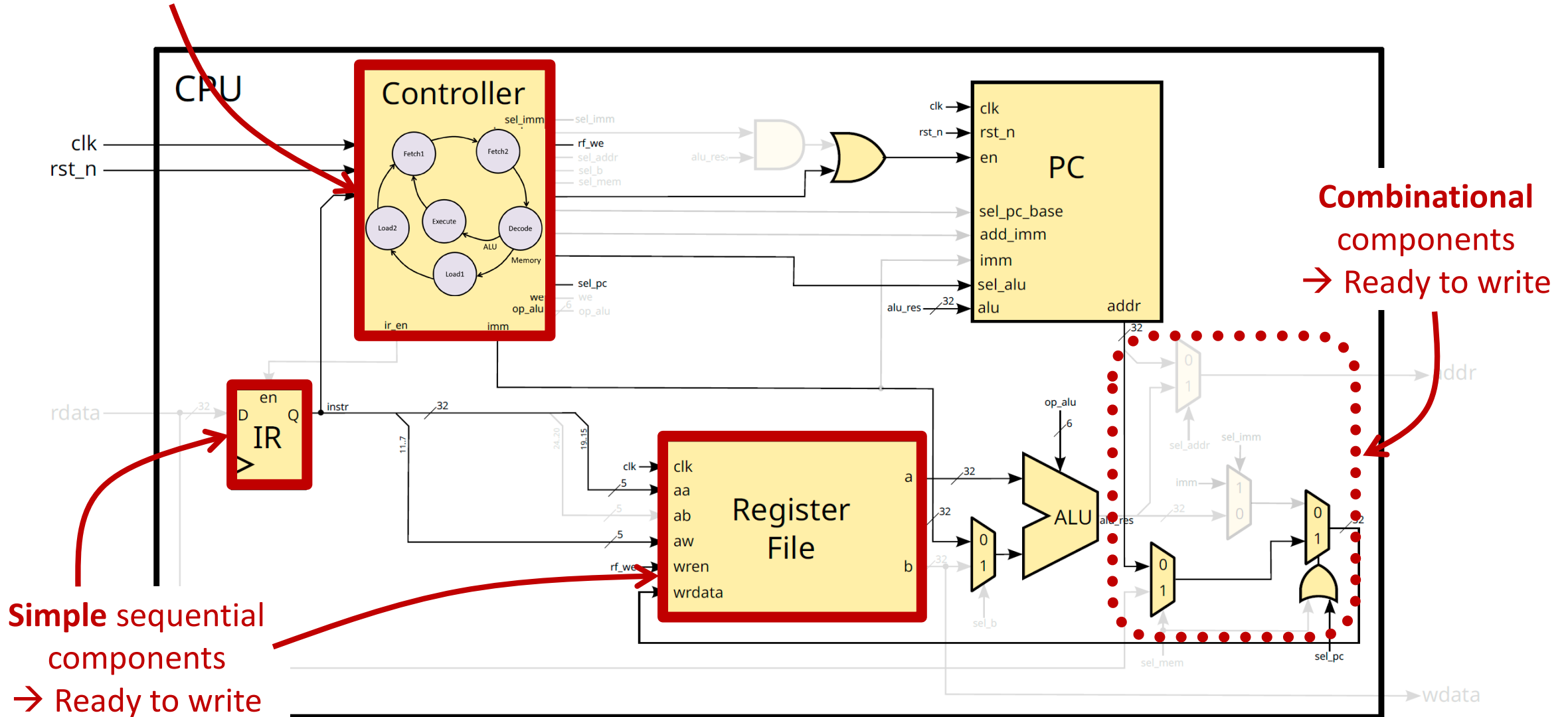

“Open the Box” of Complex Stuff

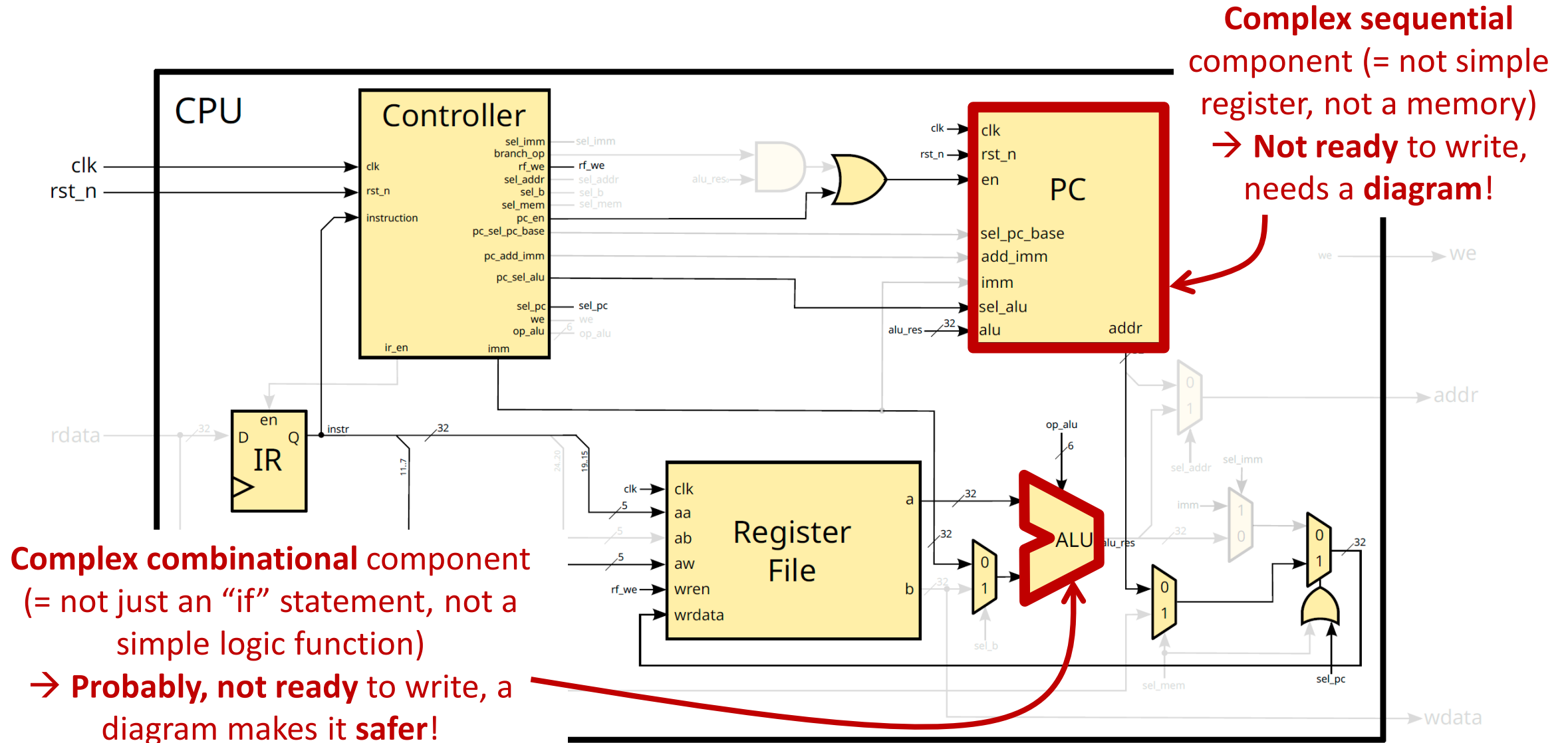

Detail Complex Combinational Modules

  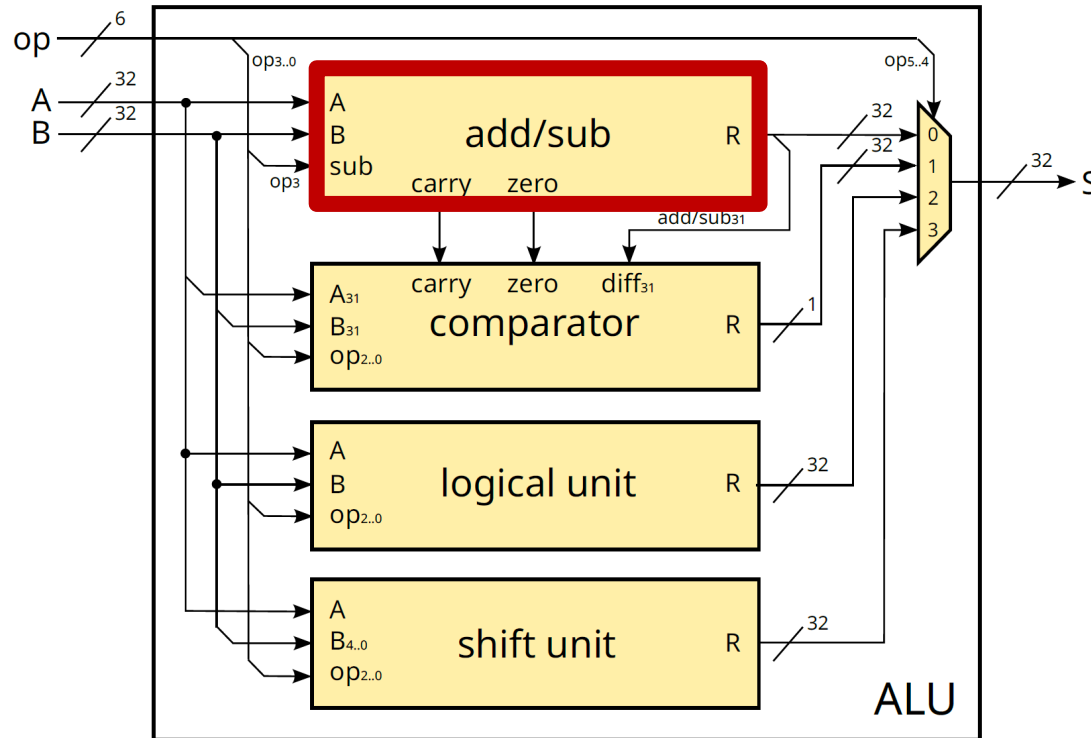  

Write Verilog by Sticking to Basic Patterns

Combinational

- **always@ (*)** is used to describe a block with combinational logic. The * symbol is used in the sensitivity list to trigger the block whenever any of the inputs are changed; therefore, the outputs reflect the inputs change.

Verilog **guidelines** in Moodle

```
always @ (*)
begin
  if (a)
    y = ~b;
  else
    y = b;
end
```

You can write **much more complex combinational** blocks (e.g., next state in FSMs)...


```
always @ (posedge clk)
begin
  if (reset == 1)
    q <= 0;
  else if ((enable1 == 1) && (enable2 == 1))
    q <= d;
end
```

...but this is just about the **most complex sequential** block you want to write!
(only **registers** and **counters**)


Sequential

- **always@ (posedge clk)** is used to describe a block with sequential logic i.e., has flip-flops. The two keywords **posedge** and **negedge** determine whether the active clock edge of the flip-flops is the rising or the falling clock edge respectively.

Three `always` Blocks per FSM, Always!

 

Mealy

 

Moore

References

- Patterson & Hennessy, COD – RISC-V Edition
 - **Chapter 4**; only **Section 4.1** to **4.5**